
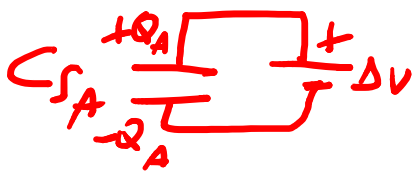


14-9-2023

P.1

CASO A

1)


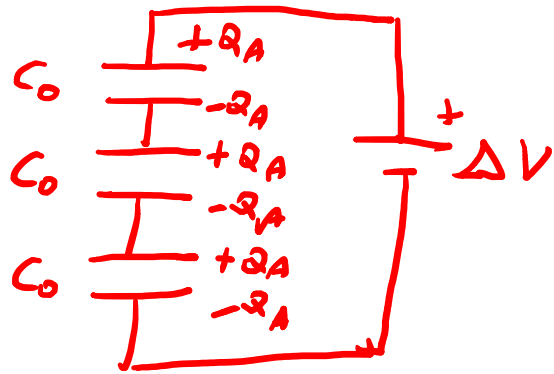


$$C_{SA} = \frac{1}{\frac{1}{C} + \frac{1}{C} + \frac{1}{C}} = \frac{C}{3}$$

$$Q_A = C_{SA} \Delta V = \frac{C}{3} \Delta V$$

$$U_A = \frac{1}{2} C_{SA} \Delta V^2 = \frac{1}{2} \frac{C}{3} \Delta V^2$$

CASO B

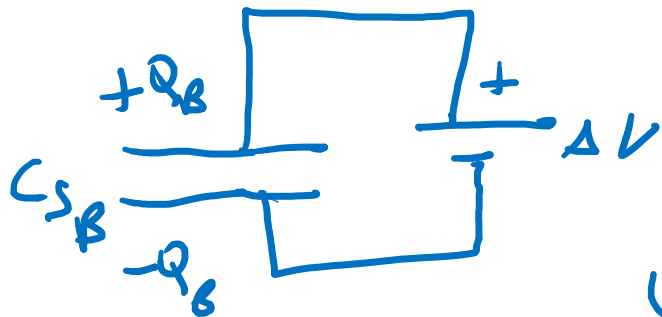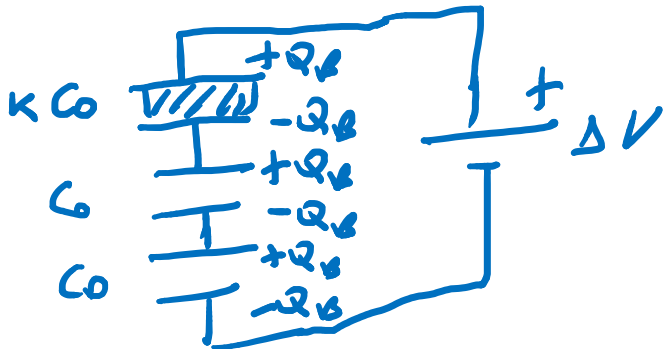

$$C_{SB} = \frac{1}{\frac{1}{kC} + \frac{1}{C} + \frac{1}{C}} = \frac{1}{\frac{1+2k}{kC}} = \frac{kC}{1+2k}$$

$$Q_B = C_{SB} \Delta V = \frac{kC \Delta V}{1+2k}$$

$$U_B = \frac{1}{2} C_{SB} \Delta V^2 = \frac{1}{2} \frac{kC}{1+2k} \Delta V^2 = \frac{4}{3} U_A$$

$$U_B = \frac{1}{2} \frac{k C_0}{1+2k} \Delta V^2 = \frac{4}{3} U_A = \frac{4}{3} \frac{1}{2} \frac{C_0}{3} \Delta V^2$$

P.2

$$\frac{4}{1+2k} = \frac{4}{9} \rightarrow 9k = 4 + 8k \rightarrow k = 4$$


LE CARICHE IN COND. INIZIALI SONO TUTTE UGUALI A $Q_B = \frac{k C_0}{1+2k} \Delta V$

OSIA CON $k = \frac{4}{4}$ $Q_B = \frac{C_0 \Delta V}{1+8} = \frac{C_0 \Delta V}{9} = \frac{C_0 \Delta V}{9}$

ENERGIA FORNITA DAL GENERATORE $U_{GEN} = \Delta V (Q_B - Q_A) = C_0 \Delta V^2 \left[\frac{k}{1+2k} - \frac{1}{3} \right] =$

CHE PER $k = \frac{4}{4}$ VIENE $U_{GEN} = C_0 \Delta V^2 \left[\frac{4}{9} - \frac{1}{3} \right] = + C_0 \Delta V^2 \left[\frac{1}{9} \right]$


2) CASO A TAPENDO

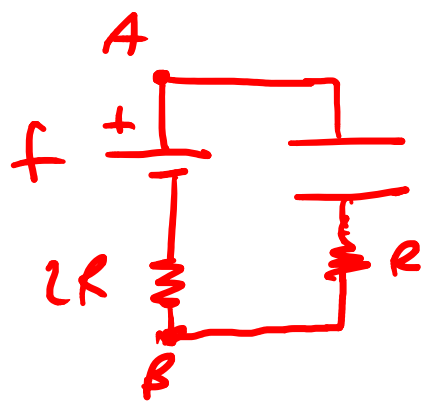

$$\Delta V_{CA} = f = V_A - V_B$$

$$Q_{CA} = C \Delta V_{CA} = C f$$

CASO B TORNANDO DA TSUP

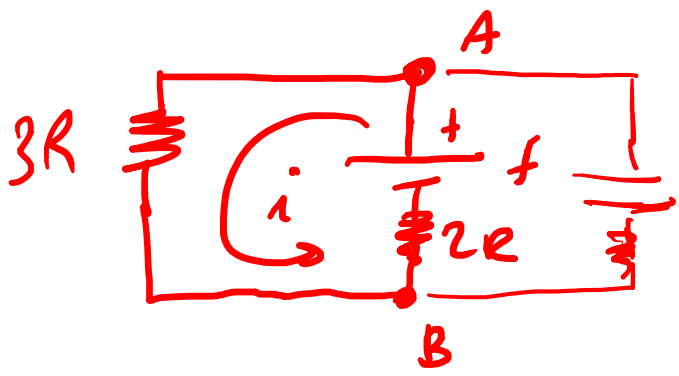

$$i = \frac{f}{5R}$$


$$\Delta V_{CB} = V_A - V_B = 3R i$$

$$\Delta V_{CB} = \frac{3R f}{5R} = \frac{3}{5} f$$

$$Q_{CB} = C \Delta V_{CB} = \frac{3}{5} C f$$

$$\Delta U = U_B - U_A = \frac{1}{2} C \Delta V_{CB}^2 - \frac{1}{2} C \Delta V_{CA}^2 = \frac{1}{2} C \left[\left(\frac{3}{5} f \right)^2 - f^2 \right] = \frac{1}{2} C f^2 \left[\frac{9-25}{25} \right] = -\frac{16}{2} C f^2$$

3)

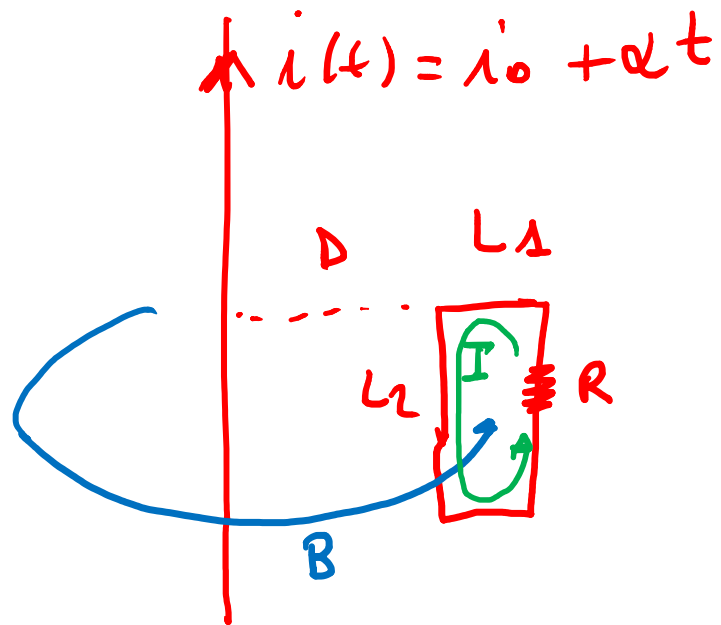

$$i(t) = i_0 + \alpha t$$

I corrente indotta

P.4

$$B(t, r) = \frac{\mu_0 i(t)}{2\pi r} = \frac{\mu_0 (i_0 + \alpha t)}{2\pi r}$$

$$\phi(B) = L_2 \int_D^{D+L_1} \frac{\mu_0 (i_0 + \alpha t)}{2\pi r} dr =$$


$$= \frac{\mu_0 (i_0 + \alpha t) L_2}{2\pi} \ln\left(\frac{D+L_1}{D}\right)$$

$$\mathcal{E}_{\text{em}} = -\frac{d\phi}{dt} = -\frac{\alpha \mu_0 L_2}{2\pi} \ln\left(\frac{D+L_1}{D}\right)$$

$$I = \frac{\mathcal{E}_{\text{em}}}{R} = -\frac{\alpha R \mu_0 L_2}{2\pi} \ln\left(\frac{D+L_1}{D}\right)$$

$$M = \frac{\phi(B)}{i(t)} = \frac{\mu_0 L_2}{2\pi} \ln\left(\frac{D+L_1}{D}\right)$$

4)

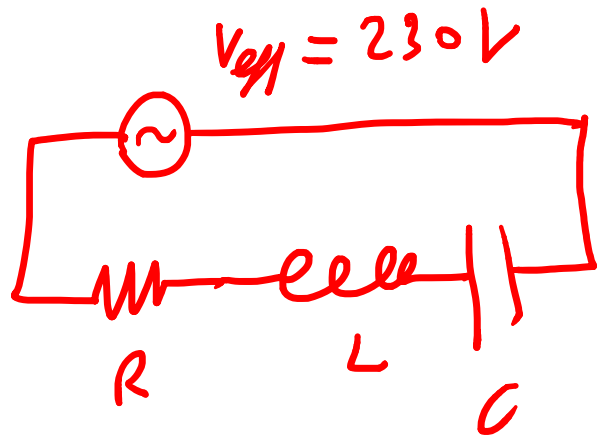

$$f = 50 \text{ Hz}$$

$$\omega = 2\pi f$$

P.5

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$i_{eff} = \frac{V_{eff}}{Z}$$

$$i_{MAX} = \sqrt{2} \cdot i_{eff}$$

$$V_{MAX} = \sqrt{2} \cdot V_{eff}$$

$$V_{MAX C} = i_{MAX} Z_C$$

$$\text{CON } Z_C = \frac{1}{\omega C}$$

$$P_m = \frac{1}{2} V_{eff} i_{eff} \cos \phi$$

$$\cos \phi = \frac{R}{Z} = \frac{R}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$