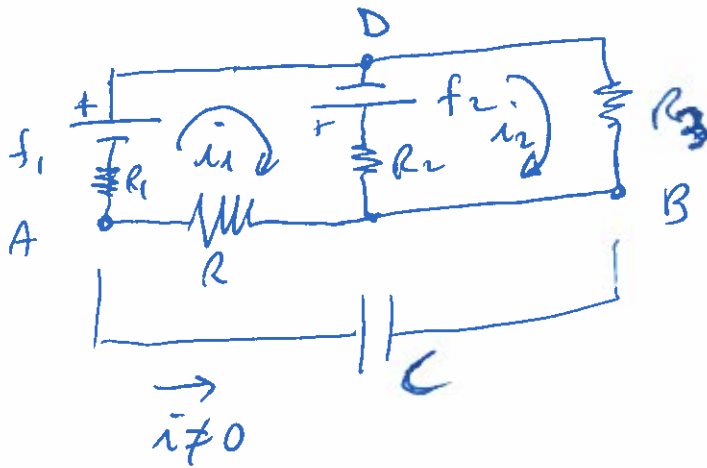


2)

IN CIRCUITO NON SCORRE CORRENTE IN R_3



$$V_C = V_{AB} = V_A - V_B$$


$$V_C = \frac{1}{2} C V_{AB}^2$$

DEVO TROVARE V_{AB} .

PER FAR SI CHE IN R_3 NON SCORRA CORRENTE

$i_2 = 0 \rightarrow$ DEVE ESSERE $V_D - V_B = 0$

è $i_2 = 0$

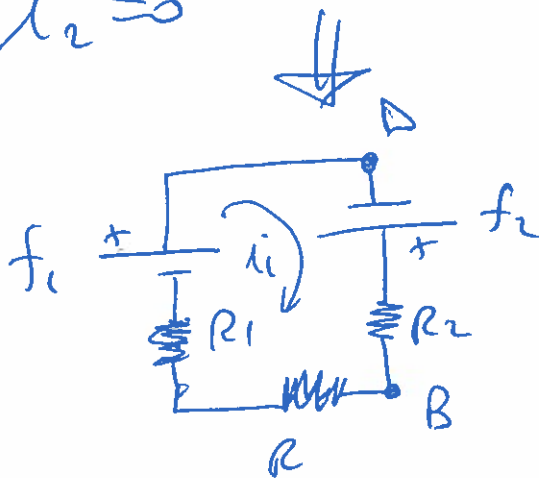

$$i = \frac{f_1 + f_2}{R_1 + R_2 + R}$$


$$V_D - V_B = -f_2 + R_2 i = 0$$

$$f_2 = R_2 i \quad i = \frac{f_2}{R_2} = \frac{f_1 + f_2}{R_1 + R_2 + R}$$

$$(R + R_1 + R_2) f_2 = R_2 (f_1 + f_2) \quad R f_2 = -f_2 (R_1 + R_2) + R_2 (f_1 + f_2)$$


$$R = R_2 \frac{(f_1 + f_2)}{f_2} - (R_1 + R_2) = \frac{f_1 R_2 + f_2 R_2 - f_2 R_1 - f_2 R_2}{f_2}$$

3)

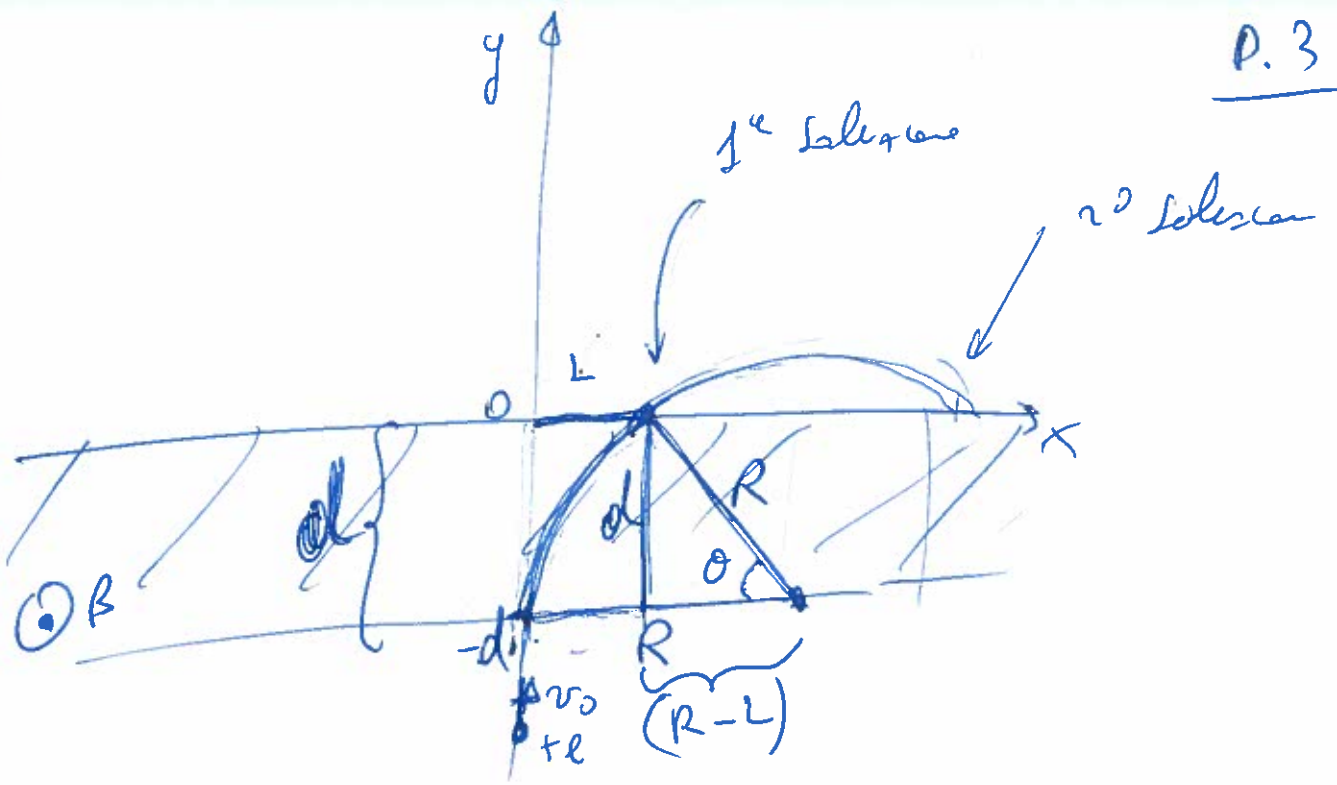

$$F = qv_0 B = m_p a_c = m_p \frac{v_0^2}{R} \quad R = \frac{m_p v_0^2}{e v_0 B} = \frac{m_p v_0}{e B}$$

per $R < d$ NON TOCCO MAI LO SCHERMO

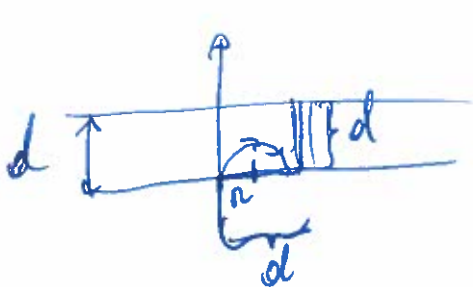

$$R = \frac{m_p v_0}{e B} < d \rightarrow B > \frac{m_p v_0}{e d}$$

Se $R \geq d$

$$R^2 = (R-L)^2 + d^2 = R^2 + L^2 - 2RL + d^2$$

$$R^2 = R^2 + L^2 - 2RL + d^2 \rightarrow L^2 - 2RL + d^2 = 0$$

$$L = \frac{2R \pm \sqrt{4R^2 - 4d^2}}{2} = R \pm \sqrt{R^2 - d^2}$$

PRENDO LO SGUARDO (-) (1^a soluzione)

$$L(B) = R - \sqrt{R^2 - d^2} = \frac{m_p v_0}{e B} - \sqrt{\frac{m_p^2 v_0^2}{e^2 B^2} - d^2}$$

$$4) i(\omega) = f_0 / \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2} \quad \text{P.6}$$

$$i_{\max} = i(\omega_0) = f_0/R \quad \text{per } (\omega_0 L - \frac{1}{\omega_0 C}) = 0 \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

$$i' = i(\omega'_0) = \frac{i_{\max}}{\sqrt{2}} = \frac{f_0}{R\sqrt{2}} = \frac{f_0}{\sqrt{R^2 + (\omega'_0 L - \frac{1}{\omega'_0 C})^2}}$$

$$2R^2 = R^2 + (\omega'_0 L - \frac{1}{\omega'_0 C})^2$$

$$(\omega'_0 L - \frac{1}{\omega'_0 C})^2 = R^2$$

$$\omega'_0 L - \frac{1}{\omega'_0 C} = \pm R \Rightarrow \omega'^2 LC - 1 \mp RC\omega' = 0$$

$$\omega' = \frac{\pm RC \pm \sqrt{R^2 C^2 + 4LC}}{2LC}$$

$\omega' \geq 0$
per cui ~~la~~ termine
con $\sqrt{\quad}$ Solo \oplus

$$\omega' = \pm \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega'_1 = +\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega'_2 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\Delta\omega = \omega'_1 - \omega'_2 = \frac{R}{2L} + \frac{R}{2L} = \frac{R}{L}$$